

Unit Name: Analogue Electronics 1 Simulation 2

Title

Rectifier Circuits

Details

The purpose of this experiment is to demonstrate the characteristics of three different diode rectifier circuits: half-wave rectifier, center- tapped full-wave rectifier, and full-wave bridge rectifier. Each type causes an ac input voltage to be converted into a pulsed waveform having an average, or dc, voltage output.